 

Submission Notes:

- This project can be done in groups of 4 students or less.
- Project grade will be based on the submitted report and cadence files; **any copied reports will be given Zero.**
- The report is limited to 15 pages without the cover, half a point will be lost for each extra page.
- The cover page must contain the group names in Arabic and their ID's.
- All graphs and figures should be clear with readable axes and traces, and all schematics of the operating points and sizing should be included.

Dead line 1 May 2025 at 11:59 PM

Q1. Using the Vm of 65nm tsmc technology, design the following amplifier to achieve the following specs:



- 1- $V_{DD} = 3.3V$
- 2- $V_{inCM} = 0.5 * V_{DD}$
- 3- ADC (DC gain) $> 58dB$
- 4- $GBW > 150MHz$ for a load capacitance of $1pF$
- 5- Slew rate $> 100 V/\mu sec$
- 6- Output swing $> 1.5 V_{PP}$
- 7- Input referred noise density $< 30nV / \sqrt{Hz}$ (include thermal and flicker only)
- 8- $PM > 60deg$
- 9- $GM > 12dB$
- 10- Minimal power consumption and area.

- Do not use ideal current sources (assume that you have only one ideal current source of $25 \mu A$ coming from V_{DD}). Use biasing circuit to generate I_1 and optimum bias for V_{b1} , V_{b2} , and V_{b3} .
- Design all current mirrors to provide close to optimum compliance voltage (to obtain maximum output swing). BUT Adjust V_{DS} of any transistor in the current mirror (or current source) to $(V_{eff} + 100 mV)$ in order to improve r_o of this transistor.

Simulations

- Simulate the circuit (DC analysis - save operating point, AC analysis)
 - Print all transistor operating point information (DC)
 - Plot the gain and phase versus frequency (AC). Show open-loop gain and PM
 - Plot the common-mode rejection ratio (CMRR)
 - Plot the power supply rejection ratio (PSRR)
 - Place the op-amp in a unity feedback (**Buffer**) configuration:
 - Simulate stability using STB analysis and IPROBE
 - Plot STB gain and phase versus frequency (AC) and calculate open-loop gain and PM –
- What is the difference between those results and previous open-loop AC results?
- Plot the DC-gain versus V_{out} (report when DC-gain drops by 10dB to verify specifications)
 -
 - Plot closed-loop (CL) frequency response. What is the ACL and BWCL (comment)?
 - Simulate input-referred noise and tabulate top 4 contributors @ 10MHz (comment).
 - Simulate the slew rate and verify the specifications.
 - Apply a sine input signal of 1Vpp @ **10 MHz** and plot V_{out} (Add proper input DC value). Plot DFT (in dB) and calculate harmonic distortion (HD2, HD3, and THD) in dB.
 - Plot V_{out} for a small step input of 100mV (Add proper input DC value). Calculate the fractional gain error (FGE) and 1% settling time (compare with hand analysis).

You are required to deliver a report that contains:

- 1- **Schematic diagrams** (snapshots from Cadence showing dimensions and values)
- 2- **Design procedure** (hand calculations)
- 3- **Simulation results** (snapshots from Cadence)
- 4- **Discussion** of your results and conclusions